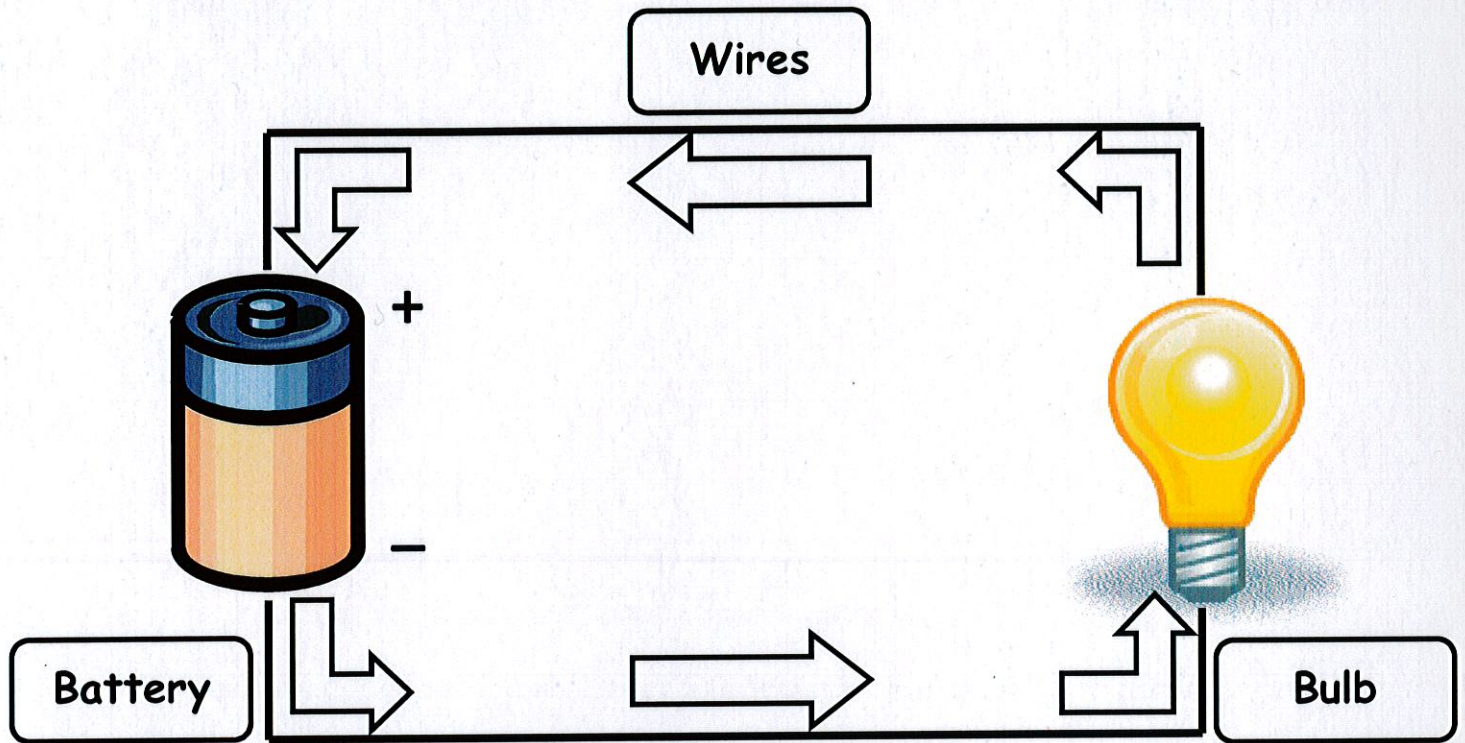


Making a Circuit

A circuit is a path that allows electricity to pass through it. For electricity to pass through the circuit must be a complete loop.



The electricity flows from the negative terminal of the battery, through the bulb and back to the positive terminal of the battery.

Electricity always flows from the negative (-) to the positive (+).